

MAE40 - Linear Circuits - Winter 25
Midterm #1, February 4

Instructions

- (i) You can use a two-sided 1-page handwritten cheatsheet.
- (ii) The exam has 2 questions for a total of 20 points and 2 bonus points.
- (iii) You have from 2:00pm to 3:20pm to do the exam, but it should require less time for you to complete it.
- (iv) You can use a calculator with no communication capabilities.
- (v) In your responses, clearly articulate your reasoning, and properly justify the steps.
- (vi) **Important:** start each part below on a separate page, use only one side, and write your name & PID at the top of each page.

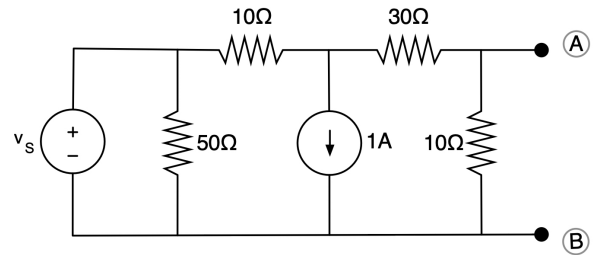


Figure 1: Circuit for question 1.

Good luck!

1. Equivalent circuits

For the circuit in Figure 1, do the following:

- Part I:** [3 points] Turn off the sources and find the equivalent resistance as seen from terminals (A) and (B).
- Part II:** [3 points] Express the open-circuit voltage as seen from terminals (A) and (B) as a function of the value v_s of the voltage source.
- Part III:** [4 points] To determine the value of v_s , an engineer connected a $R = 16 \Omega$ resistor to terminals (A) and (B) and measured the power supplied to R as $\frac{1}{9} W$. They then used this information and the fact that $v_s \neq 0$ to find out the value of v_s . What is it?
- Part IV:** [Extra 2 points] Instead, when the engineer connected a fuse rated at $50 mA$ and a $R = 16 \Omega$ resistor in series to terminals (A) and (B), they measured the power supplied to R as $0 W$. Why?

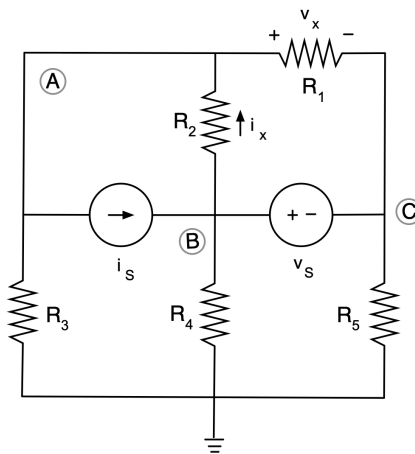


Figure 2: Circuit for question 2.

2. Circuit analysis

- Part I:** [6 points] Formulate node-voltage equations for the circuit in Figure 2. Use the node labels provided. Clearly indicate the final equations and circuit variable unknowns. Write the final equations **in matrix form** in the unknown node-voltages. **Do not modify the circuit or the labels.** No need to solve any equations!
- Part II:** [2 points] Provide expressions for the voltage v_x and the current i_x in terms of node voltages.
- Part III:** [2 points] Among the choices for ground other than the bottom node, are there any that are better? Why?